


connect to positive of voltage supply

connect power to bridge

Measure the bridge output voltage across b and c

All these dots near the red line are now the ground

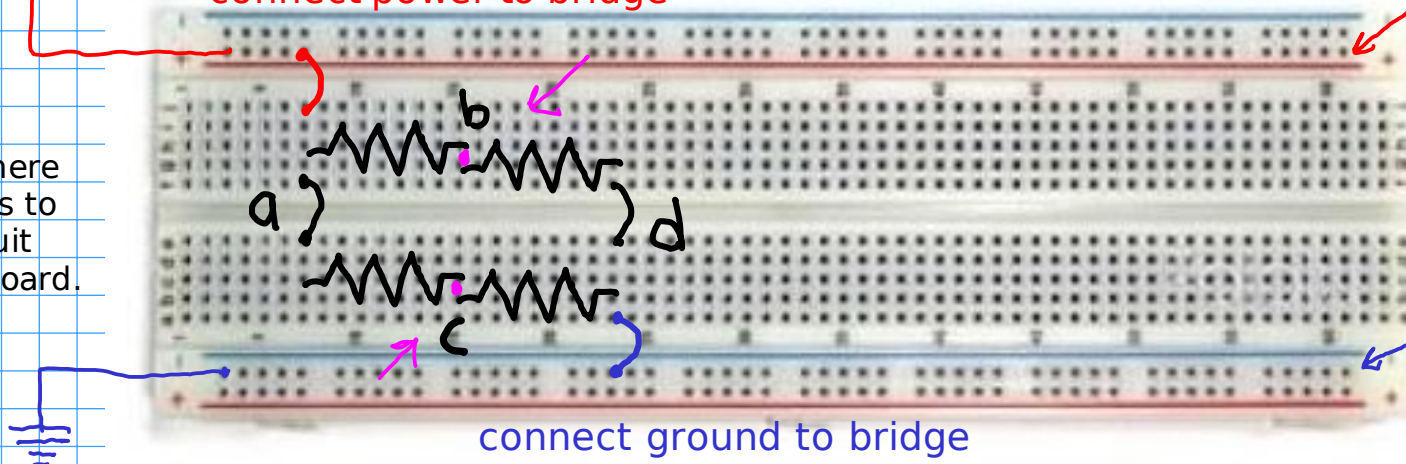This is just a suggestion. There are many ways to build this circuit on the breadboard.



connect ground to bridge

All these dots near the blue line are now the ground

Connect to negative of voltage supply