

Module 7 - Strain Gauges

ME3023 - Measurements in Mechanical Systems

Mechanical Engineering

Tennessee Technological University


Topic 2 - The Wheatstone Bridge

Topic 2 - The Wheatstone Bridge

- Resistive Gauges
- The Bridge Circuit
- Balancing the Bridge
- Gauge Sensitivity

Resistive Gauges

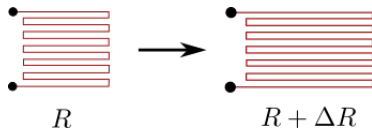The resistive strain gauge, aka _____, is bonded to the surface so that it deforms with the specimen. The change in length of the bonded gauge causes a change in resistance which is used as a _____.




Images: T.Hill

Resistive Gauges


The _____ is typically used instead of the physical parameters.

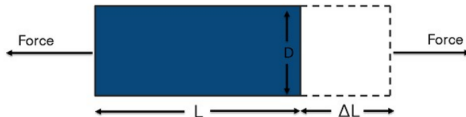This number relates the relative change in resistance to the measured strain.



Images: NI

The Bridge Circuit

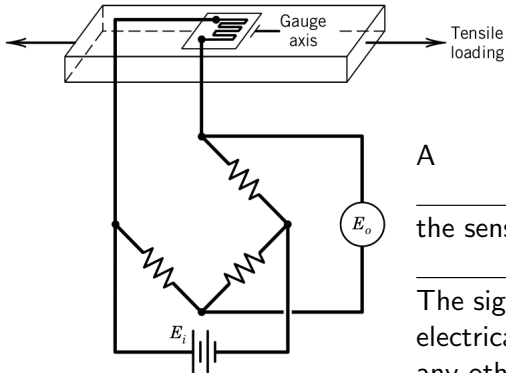


A

_____ converts
the sensed information into a

The signal might be mechanical,
electrical, optical, or may take
any other form that can be
meaningfully recorded.

The Bridge Circuit

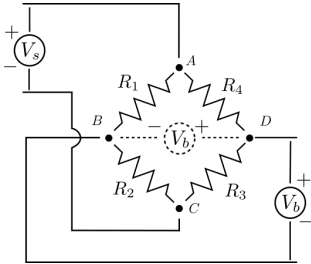


Images: T.Hill

How does the bridge circuit work as a transducer?

Use KVL and the voltage divider rule find the relationship between the two voltages.

Balancing the Bridge

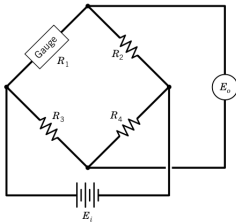
If all four resistors are equal the bridge voltage will equal zero and the bridge is said to be **balanced**. One or more resistors in the circuit is replaced by a strain gauge and bridge voltage is used as a measure of change in resistance and therefore strain.



This gives a linear **calibration curve** with a convenient **zero offset**.

Text. Images: Theory and Design for Mechanical Measurements

Gauge Sensitivity

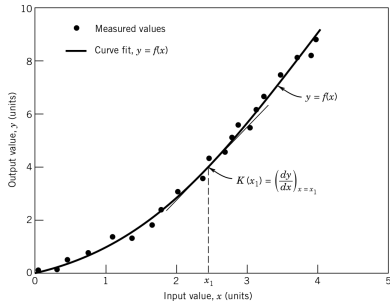

Assume $R = 120\Omega$ for all resistors and the bridge is balanced in a condition of zero strain. What is the **static sensitivity** of the gauge and bridge circuit described?

$K =$

Text. Images: Theory and Design for Mechanical Measurements

Gauge Sensitivity

Gauge Sensitivity