Module 7 - Time Varying Circuits

ME3023 - Measurements in Mechanical Systems

Mechanical Engineering
Tennessee Technological University

Topic 1 - The Constitutive Equations

Topic 1 - The Constitutive Equations

- —
- —
- —
- —

_

Passive components affect the behavior of a circuit in different ways but they do not generate power and can only absorb energy or transform it into heat. Active components on the other hand...

- Resistor
- Capacitor
- Inductor


Most circuits require an active power source for operation. A voltage source is used in most applications however current sources are also available and are needed for specialized electrical applications.

Components are identified by color codes and numbering systems. However it is always a good idea to measure for yourself because a marking can be incorrect or a component may be damaged.

	Re	sistor C	Color Co	ode		
4 band (looser	s resistor tolerance)	with +/-			60k Ω 10% tolerance	
	ds resistor wer tolerance)			23: with +/- 19	7 Ω 6 tolerance	
	_	ים ו נ	\neg			
Color	1™ Band	2 nd Band	3 rd Band	Multiplier	Tolerance	
Black	0	0	0	x1Ω		
Black Brown	0			x 1 Ω x 10 Ω	+/- 1%	
Black Brown Red	1 2	1 2	1 2	x 1 Ω x 10 Ω x 100 Ω		
Black Brown Red Orange	0 1 2 3	0 1 2 3	1 2 3	×1Ω ×10Ω ×100Ω ×1KΩ	+/- 1%	
Black Brown Red Orange Yellow	0 1 2 3 4	0 1 2 3 4	0 1 2 3 4	x 1 Ω x 10 Ω x 100 Ω x 1K Ω x 10K Ω	+/- 1%	
Black Brown Red Orange Yellow Green	0 1 2 3 4 5	0 1 2 3 4 5	0 1 2 3 4 5	× 1 Ω × 10 Ω × 100 Ω × 1 K Ω × 10 K Ω × 100 K Ω	+/- 1% +/- 2% +/- 5%	
Black Brown Red Orange Yellow Green Blue	0 1 2 3 4 5	0 1 2 3 4 5	0 1 2 3 4 5	×1 Ω ×10 Ω ×100 Ω ×1KΩ ×10KΩ ×100KΩ ×100KΩ	+/- 1% +/- 2% +/5% +/25%	
Black Brown Red Orange Yellow Green Blue Violet	0 1 2 3 4 5 6	0 1 2 3 4 5 6	0 1 2 3 4 5 6 7	× 1 Ω × 10 Ω × 100 Ω × 1 K Ω × 10 K Ω × 100 K Ω	+/- 1% +/- 2% +/- 3% +/- 25% +/- 1%	
Black Brown Red Orange Yellow Green Blue Violet Grey	0 1 2 3 4 5 6 7	0 1 2 3 4 5 6 7	0 1 2 3 4 5 6 7	×1 Ω ×10 Ω ×100 Ω ×1KΩ ×10KΩ ×100KΩ ×100KΩ	+/- 1% +/- 2% +/5% +/25%	
Color Black Brown Red Orange Yellow Green Blue Violet Grey White Gold	0 1 2 3 4 5 6	0 1 2 3 4 5 6	0 1 2 3 4 5 6 7	×1 Ω ×10 Ω ×100 Ω ×1KΩ ×10KΩ ×100KΩ ×100KΩ	+/- 1% +/- 2% +/- 3% +/- 25% +/- 1%	

www.circuitspedia.com								
Picofarad	Nanofarad	Microfarad		Picofarad	Nanofarad	Microfarad		
pF	nF	μF	CODE	pF	nF	μF	CODE	
10	0.01	0.00001	100	4700	4.7	0.0047		
15	0.015	0.000015		5000	5.0	0.005		
22	0.022	0.000022		5600	5.6	0.056		
33	0.033	0.000033		6800	6.8	0.0068	682	
47	0.047	0.000047		10000	10	0.01		
100	0.1	0.0001		15000	15	0.015		
120	0.12	0.00012		22000	22	0.022		
130	0.13	0.00013		33000	33	0.033		
150	0.15	0.00015		47000	47	0.047		
180	0.18	0.00018		68000	68	0.068		
220	0.22	0.00022		100000	100	0.1	104	
330	0.33	0.00033		150000	150	0.15		
470	0.47	0.00047		200000	200	0.2		
560	0.56	0.00056		220000	220	0.22		
680	0.68	0.00068	681	330000	330	0.33		
750	0.75	0.00075		470000	470	0.47		
820	0.82	0.00082		680000	680	0.68	684	
1000	1.0	0.001		1000000	1000	1.0		
1500	1.5	0.0015		1500000	1500	1.5		
2000	2.0	0.002		2000000	2000	2.0	205	
2200	2.2	0.0022		2200000	2200	2.2		
3300	3.3	0.0033		3300000	3300	3.3		

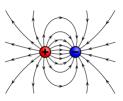 Charge - the physical property of matter that causes it to experience a force when placed in an electromagnetic field.



- Voltage the difference in electric potential between two points ... can be caused by electric charge, by electric current through a magnetic field, by time-varying magnetic fields, or some combination of these three.
- Current the rate of flow of electric charge past a point or region. An electric current is said to exist when there is a net flow of electric charge through a region.


_

- Resistance a measure of a components opposition to the flow of electric current. The inverse quantity is electrical conductance, and is the ease with which an electric current passes.
- Capacitance the ratio of the change in electric charge of a system to the corresponding change in its electric potential (voltage).
- Inductance the tendency of an electrical conductor to oppose a change in the electric current flowing through it. The flow of electric current creates a magnetic field around the conductor. The field strength depends on the magnitude of the current, and follows any changes in current.

Quantity	Symbol	Unit	Abbr.
Charge	Q,q	Coulomb	С
Voltage	V,v	Volt	V
Current	I,i	Ampere	А
Resistance	R	Ohm	Ω
Capacitance	С	Farad	F
Inductance	L	Henry	Н

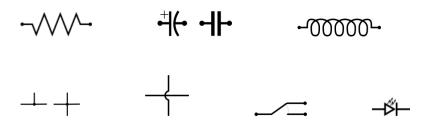Question: When should you use upper case or lower case letters for electrical quantities?

When working with a or building a circuit you need a diagram. Draw or find one before you begin. Here are some commonly used symbols.



_

A switch is a mechanical-electrical device that that can change from a continuous state to a dis-continuous state and they are used as a mechanical interface to a circuit. There many different types of switches for different purposes and this is not an exhaustive list.

- Toggle Switches
- Momentary Switches
- Reed Switches
- Level or Float Switches
- and many more

Toggle switches are are possibly the most commonly used switches and they come in many different forms.

Poles - The numbers of poles refers to the number of independent conductors or circuits in a switch that are controlled by the same toggle or input.

Throws - The numbers of throws refers to the number of output terminals of a switch per pole.

