

## Module 4 - Steady State Circuits

ME3023 - Measurements in Mechanical Systems

Mechanical Engineering  
Tennessee Technological University

### Topic 2 - Fundamental Laws

## Topic 2 - Fundamental Laws

- Ohm's Law
- Combining Resistance
- Kirchhoff's Laws
- Power Dissipation

# Ohm's Law


James Maxwell



George Ohm



Ohm's Notebook

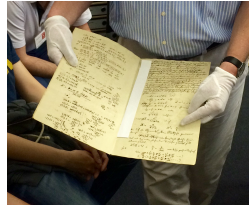

Ohm did his work on resistance in the years 1825 and 1826, and published his results in 1827 as the book *Die galvanische Kette, mathematisch bearbeitet*...


# Ohm's Law

Ohm's law states that the current through a conductor between two points is directly proportional to the voltage across the two points.




# Combining Resistance

## Resistors in Series

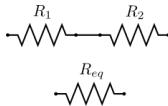

## Resistors in Parallel

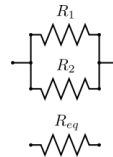

# Kirchhoff's Laws

Both of Kirchhoff's laws can be understood as corollaries of Maxwell's equations in the low-frequency limit. They are accurate for DC circuits, and for AC circuits at frequencies where the wavelengths of electromagnetic radiation are very large compared to the circuits.


1

2

# Kirchhoff's Laws

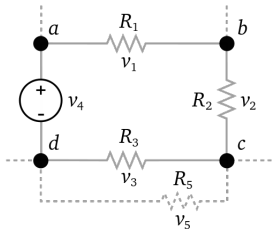
## Kirchhoff's Voltage Law (KVL) -

The sum of the voltages around a loop (aka mesh) equals zero.


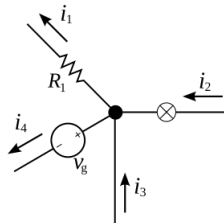
## Kirchhoff's Current Law (KCL) -

The sum of the current flowing in and out of node (aka junction) equals zero.



# Power Dissipation

Energy is transformed in to heat in passive circuit components. For a resistor the power dissipation can be found with following relations.



# Power Dissipation

Power is the rate of energy dissipated, aka the amount of energy lost per unit of time. How do we compute total energy for the power?