

Module 6 - Steady State Circuits

ME3023 - Measurements in Mechanical Systems

Mechanical Engineering

Tennessee Technological University


Topic 2 - Fundamental Laws

Topic 2 - Fundamental Laws

- Ohm's Law
- Kirchhoff's Laws
- Power Dissipation
- Example: Resistance Sensor

Ohm's Law

George Simon Ohm

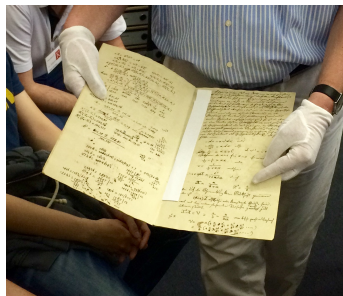

Ohm did his work on resistance in the years 1825 and 1826, and published his results in 1827 as the book *Die galvanische Kette, mathematisch bearbeitet*...


Ohm's Law

Ohm's law states that the current through a conductor between two points is directly proportional to the voltage across the two points.

$$I = \frac{V}{R}$$

It is more commonly shown in the following form.

$$V = IR$$

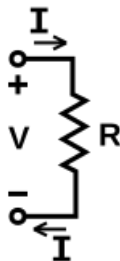

Kirchhoff's Laws

Both of Kirchhoff's laws can be understood as corollaries of Maxwell's equations in the low-frequency limit. They are accurate for DC circuits, and for AC circuits at frequencies where the wavelengths of electromagnetic radiation are very large compared to the circuits.


- 1 Kirchhoff's Voltage Law (KVL)
- 2 Kirchhoff's Current Law (KCL)

Kirchhoff's Laws

Kichhoff's Voltage Law

(KVL) - The sum of the voltages around a loop (aka mesh) equals zero.


$$\sum_{k=1}^n V_k = 0$$

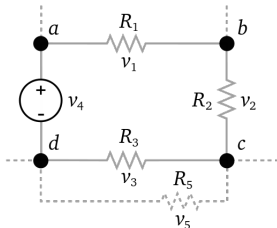

Kichhoff's Current Law

(KCL) - The sum of the current flowing in and out of node (aka junction) equals zero.

$$\sum_{k=1}^n I_k = 0$$

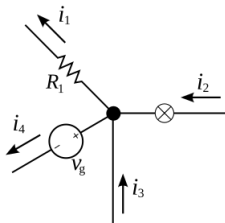

Power Dissipation

Energy is transformed in to heat in passive circuit components. For a resistor the power dissipation can be found with following relations.

$$P = IV$$

$$V = IR$$


Power Dissipation

Power is the rate of energy dissipated, aka the amount of energy lost per unit of time. How do we compute total energy for the power?

$$E = \int_{t1}^{t2} P dt$$

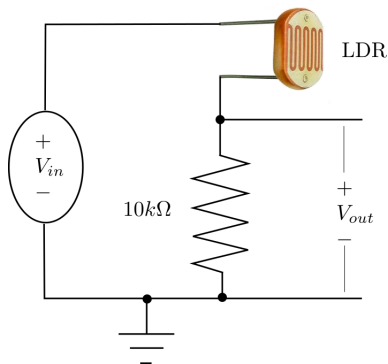Example: Resistance Sensor

Consider the simple circuit shown for measuring light intensity.



- 1 Find the current in the loop.
- 2 Find the voltage drop across the LDR.
- 3 Find the voltage drop across the $10k\Omega$ resistor.
- 4 Find the power dissipated the resistor and the total energy lost to heat over 10 seconds.

Example: Resistance Sensor